

C21, C24, C25, C27, C28, C29, C30, C32, C35, C37, C44, C45, C49, C52, C53 = 100n (assumed)

Modelling indicates motor current range of 0 to 24A  
gives an output (IV) voltage range of 0 - 3.2V  
(Motor rated 0-10.5A)

Similarly, MV ranges 0- 3.6V for  
voltage range of 0 - 200V  
(Motor rated for 180V)

Motor control and protection :-  
Power turned on, charges caps through R55.  
SMPS controller starts providing power to PIC and treadmill user control panel  
HV voltage increases to 3.6V as caps charge (ie to ~320V DC or caps fully charged)  
PIC allows RLA2 to close through PIC pin 10  
User clicks power switch which causes RLA2 to close its contacts and PIC reads this through PIC pin 9  
PIC starts motor PWM based on user selected speed, measures RPM, HV, IV and MV.  
If MV > 180V - trip motor (excess voltage ie speed )  
If MV < 0V - trip motor as motor is generating  
If HV > 3.6V - trip motor as excessive Input voltage  
If HV < 3.6V - trip motor as excessive current being drawn or something wrong with the incoming supply  
If IV > 2V then motor overloaded as motor current > 10.5A  
IV may exceed 2V to 3.2V (24A) for brief periods - say when a large user steps onto the treadmill belt so IV should have a 1s or so time delay before it trips the motor If the treadmill belt is heavily loaded the PWM duty cycle is high, then the user suddely steps off, the motor will speed up instantly, so IV suddenly falls but the RPM rises quickly

So HV and IV are analog inputs and MV can be analog or an interrupt, likely analog for PID reasons

RPM is not sensed by an interrupt capable pin, so it must be polled.


LTspice model indicates (resistive load)  
IV rises with rising load current - 2V @10ohm, 1.3V @ 30ohm  
MV rises decreasing load current - 4.5V @ 30ohm, 2.8V @ 10ohm  
HV rises with increasing load current - 4.2V @ 10ohm, 2V @ 10ohm


Note: Not guaranteed to be correct. Use at your own risk.  
PF906 DC Motor driver schematic reproduced by Happymacer



Sheet: /  
File: copy redrawn pf906 dc motor driver board.sch

**Title:** PF906 treadmill DC Power schematic

Size: A3	Date: 23/5/2021	Rev: 1
KiCad E.D.A. eeschema (5.1.9)-1		Id: 1/6

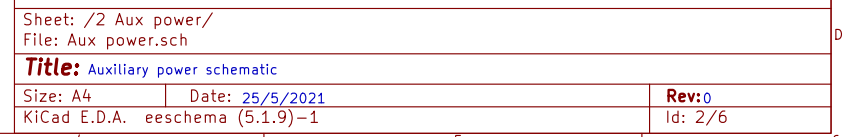

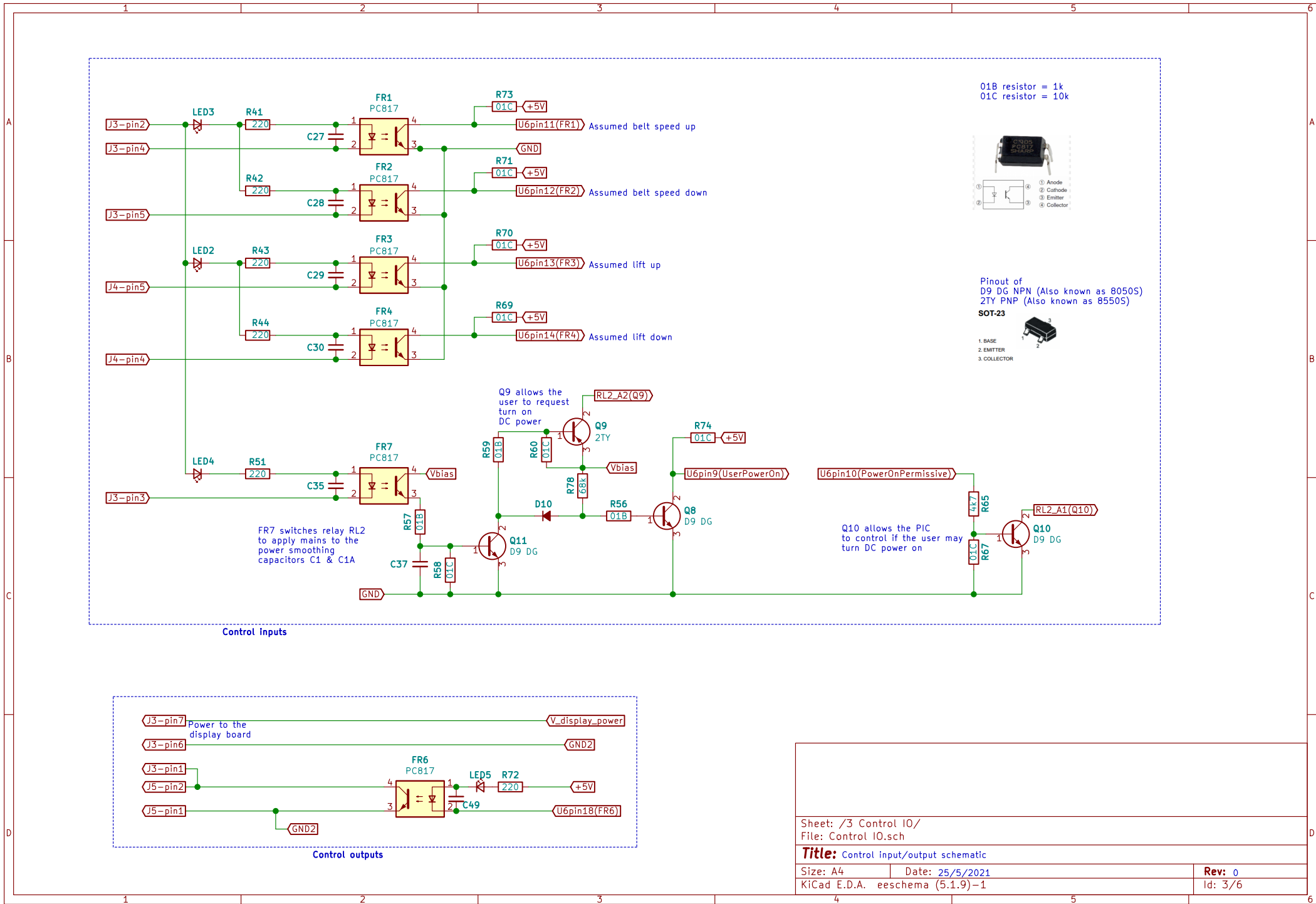

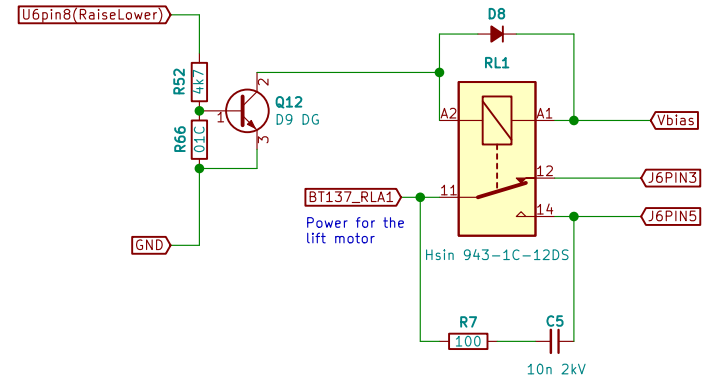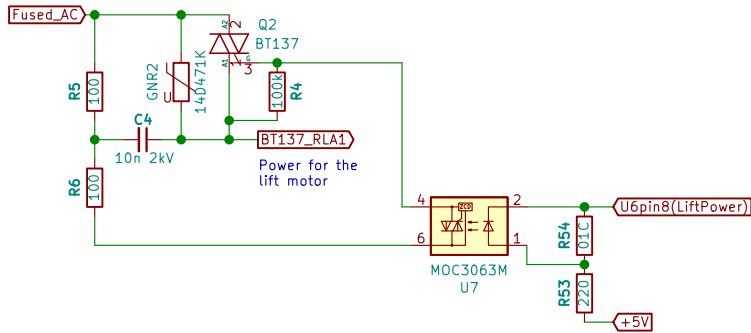


**Title:** Lift motor power schematic

KiCad E.D.A. eeschema (5.1.9)–1

KiCad E.D.A. eeschema (5.1.9)–1

Id: 4/6

RPM sensor

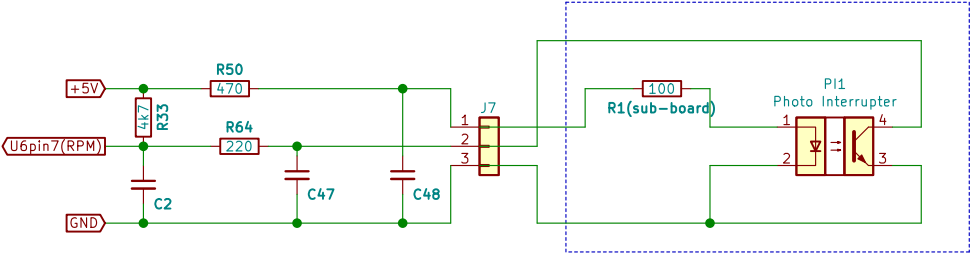

Daughter board mounted on motor across a disk mounted on the motor shaft.  
The disk has 36 slots and same number of spaces between slots.  
Max motor speed is 4700RPM so max pulse rate is  $4700 \cdot 36 / 60 = 2820\text{Hz}$

RPM is not sensed by an interrupt capable pin, however it does connect to the inverting input of either Comparator 1 or Comparator 2 of the PIC chip. Either comparator can generate an internal interrupt.

Consider that when a hole in the disk moves to expose the LED. As the hole approaches the light level increases, reaches a peak then drops again. Much like a typical day, where the sun rises at dawn and sets at dusk but its not an abrupt light level change. Pushing the light signal through a compartor therefore makes sense to square off the wave and trigger on the rising or falling edges of the wave.

Counting the pulses from this wave is thus simplified by using a comparator in the PIC.

